

Q.P. Code : 11124

**First Semester B.Sc. Degree Examination,
November/December 2019**

(CBCS Scheme – Freshers & Repeaters (Common))

Electronics

Paper I – BASIC ELECTRONICS

Time : 3 Hours]

[Max. Marks : 70

Instructions to Candidates :


- 1) Answer all questions from Part-A, any Five from Part-B and any Four from Part-C.
- 2) Answer all questions of Part-A in any one page, the same questions answered multiple times will not be considered for evaluation.

PART – A

Answer all the sub-divisions :

(15 × 1 = 15)

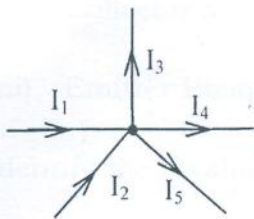1. (a) In a step down transformer, the number of turns in the secondary coil is
 - (i) less than primary coil turns
 - (ii) more than primary coil turns
 - (iii) equal to primary coil turns
 - (iv) none of the above.
- (b) Higher the Q factor of a resonant circuit
 - (i) Smaller the bandwidth
 - (ii) Larger the bandwidth
 - (iii) Smaller the resonant frequency
 - (iv) Larger the resonant frequency.
- (c) When KCL is applied to the node shown in figure, the equation is




- (i) $I_1 + I_2 - I_3 - I_4 - I_5 = 0$
- (ii) $I_1 + I_5 + I_4 - I_2 - I_3 = 0$
- (iii) $I_1 - I_2 + I_3 + I_4 - I_5 = 0$
- (iv) $I_1 - I_2 - I_3 - I_4 - I_5 = 0$.

Q.P. Code : 11124

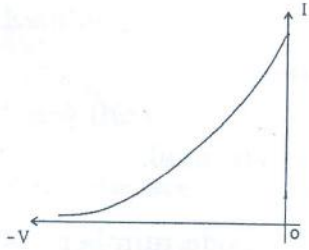- (d) Super position theorem can be applied only to circuits having
- (i) Resistive elements
 - (ii) Passive elements repeat
 - (iii) Non-linear elements
 - ~~(iv)~~ Linear bilateral elements.
- (e) A constant current source with a resistance in a parallel represents
- ~~(i)~~ Norton's equivalent circuit
 - (ii) Thevenin's equivalent circuit
 - (iii) Kirchhoff's equivalent circuit
 - (iv) Millman's equivalent circuit.
- (f) Third approximation of a diode is represented by
- (i) dc source with a series ideal diode
 - (ii) only a series resistance
 - (iii) only an ideal diode
 - ~~(iv)~~ dc source with ideal diode and a resistance.
- (g) Which of the following is not an essential element of a d.c. power supply
- (i) filter
 - (ii) rectifier
 - ~~(iii)~~ voltage regulator
 - (iv) voltage amplifier.
- (h) In a centre tapped Full wave Rectifier, if the peak voltage across each section in the secondary of the transformer is 100 V, PIV appearing across each diode is
- (i) 100 V
 - (ii) 200 V
 - (iii) 300 V
 - ~~(iv)~~ 50 V.
- (i) In a Bipolar Junction Transistor
- ~~(i)~~ Emitter is moderate in size and heavily doped
 - (ii) Emitter is larger in size and heavily doped
 - (iii) Emitter is smaller in size and heavily doped
 - (iv) Emitter is smaller in size and lightly doped.

Q.P. Code : 11124

(j) The which device exhibits the following transfer characteristics is




- (i) Diode
- (ii) BJT
- ~~(iii) Zener diode~~
- (iv) JFET.

(k) When the collector-base junction in transistor is reverse biased and the emitter-base junction is forward biased, the transistor is said to be in the

- ~~(i) active region~~
- (ii) cut-off region
- (iii) saturation region
- (iv) switching region.

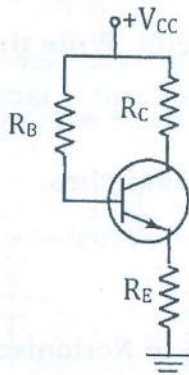(l) The biasing circuit shown here is _____



- (i) Collector to base Bias
- (ii) Voltage divider Bias
- (iii) Emitter Bias
- ~~(iv) Fixed bias with emitter feedback.~~

(m) Identify the invalid BCD number in the following

- (i) 1001
- (ii) 1111
- ~~(iii) 1000~~
- (iv) 0111.

Q.P. Code : 11124

- (n) The code used in digital systems to represent decimal digits, alphabets and other special characters such as +, -, *, etc. is
- (i) EBCDIC (ii) Gray
(iii) BCD (iv) Hexadecimal.
- (o) Next consecutive number in the array of Gray code numbers 0000, 0001, 0011 is
- (i) 0010 (ii) 0110
(iii) 0111 (iv) 1110.

PART - B

Answer any **FIVE** questions :

(5 × 7 = 35)

2. (a) Explain the method of conversion of a voltage source into a current source.
(b) Explain with a circuit, growth of charge in a series RC circuit. Show it graphically and define 'time constant'. **(2 + 5)**
3. (a) Draw the circuit diagram of a parallel resonance circuit. Write the condition for Resonance and expressions for resonant frequency and Q factor.
(b) Draw the circuit symbols for SPDT, DPST and DPDT switches. **(4 + 3)**
4. (a) State Super position theorem.
(b) With the help of circuit diagrams, explain the steps to Nortonise a resistive network. **(2 + 5)**
5. (a) Draw the block diagram of a regulated power supply.
(b) With a circuit diagram, explain the working of a Zener diode as a voltage Regulator. **(2 + 5)**
6. (a) With a circuit diagram, explain the operation of a Shunt capacitor filter.
(b) Draw the circuit of a centre tapped full wave rectifier. **(5 + 2)**


Q.P. Code : 11124

7. (a) With a relevant diagram, explain the working of an NPN Transistor.
(b) Establish the relation between ' α ' and ' β ' for a transistor. (5 + 2)
8. (a) Draw the circuit of a Darlington pair transistor and write its applications.
(b) Write the need for biasing. Define the term "Stability factor". (3 + 4)
9. (a) Explain with example, method to convert a decimal number into its Hexadecimal Equivalent.
(b) Write the Excess 3 and Gray code equivalents for all the Decimal digits. (3 + 4)

PART - C

Answer any **FOUR** questions : (4 × 5 = 20)

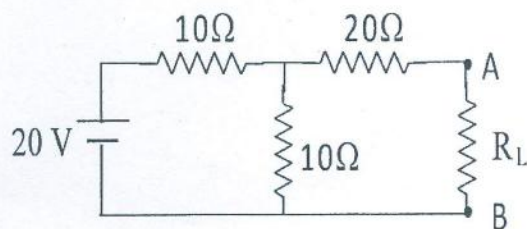10. A series resonance circuit has a capacitor of 220 pF, an inductor of 50 μH and a resistor of 10 Ω . Calculate :
(a) resonant frequency
(b) band width when Q factor is 200.
11. Determine value of R_L for Maximum power transfer in the following circuit. Also calculate the Maximum power delivered to the load.




12. In a half-wave rectifier circuit the input voltage is 220 V and the transformer ratio is 10 : 1. Determine :
(a) Dc output voltage and
(b) PIV. Assume the diode as ideal.

Q.P. Code : 11124

13. Draw the D.C. load line and mark the operating point for the biasing circuit shown.

Given : $\beta = 200$.

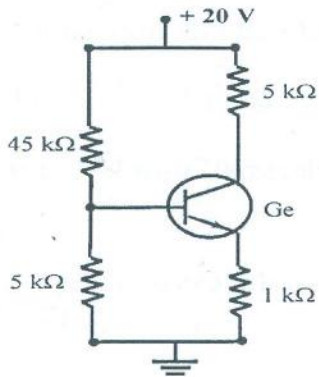

14. (a) Subtract $3F_{(16)}$ from $2D_{(16)}$ using 2's complement method.
(b) Add $10001_{(2)}$ with $1001_{(2)}$ (3 + 2)
15. (a) Convert the following binary numbers into decimal
(i) $110101001_{(2)}$ (ii) $1100111_{(2)}$
(b) Subtract $C9_{(16)}$ from $FF_{(16)}$. Express the result in Binary. (2 + 3)
-